

# CMOS Inverter Layout

**Name:** Sparsh Arya

**Registration Number:** 17BEC0656

**Lab slot:** L37 + L38

## **Aim**

- To draw the schematic of inverter
- To draw the layout of inverter
- To remove any errors caused
- To check its functionality
- To calculate Delay


## **Materials required**

### Cadence Software


- Gnd
- Vdc
- NMOS
- PMOS
- Vdd
- Vpulse
- Input and Outputs

## Observations


### 1. Drawing the Schematic in Virtuoso

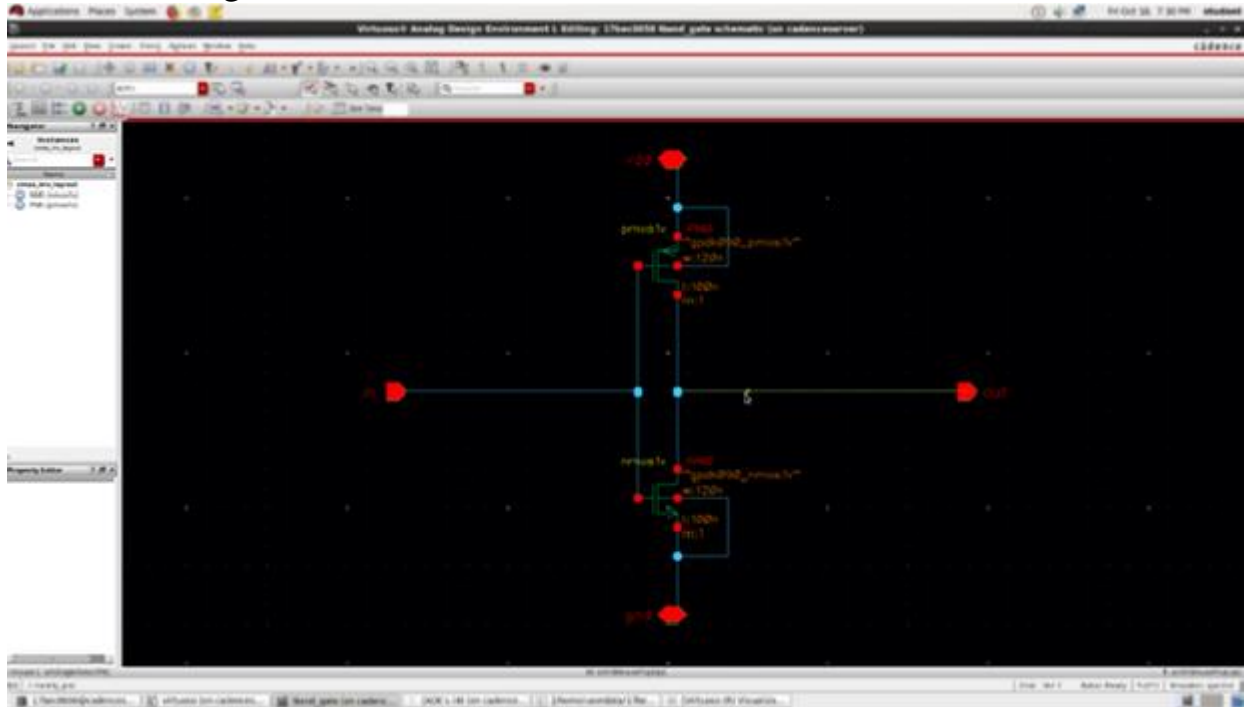


### 2. Drawing the layout in Layout XL

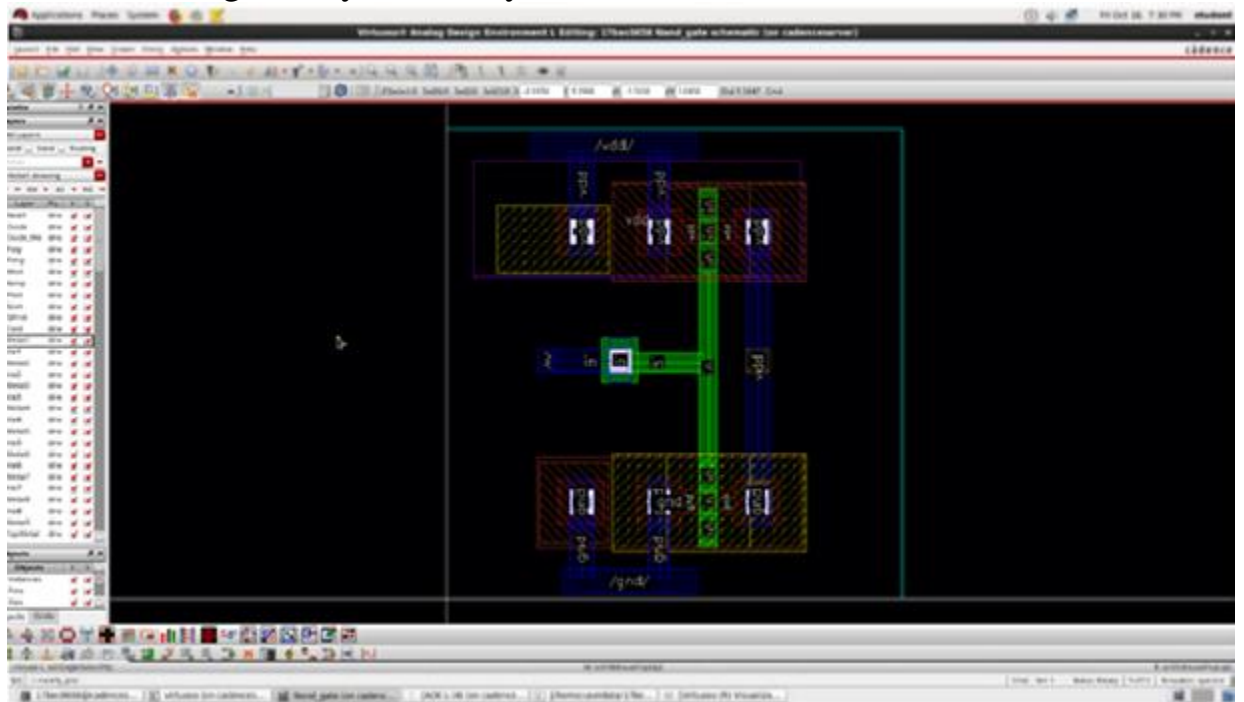


### 3. Removing DRC error

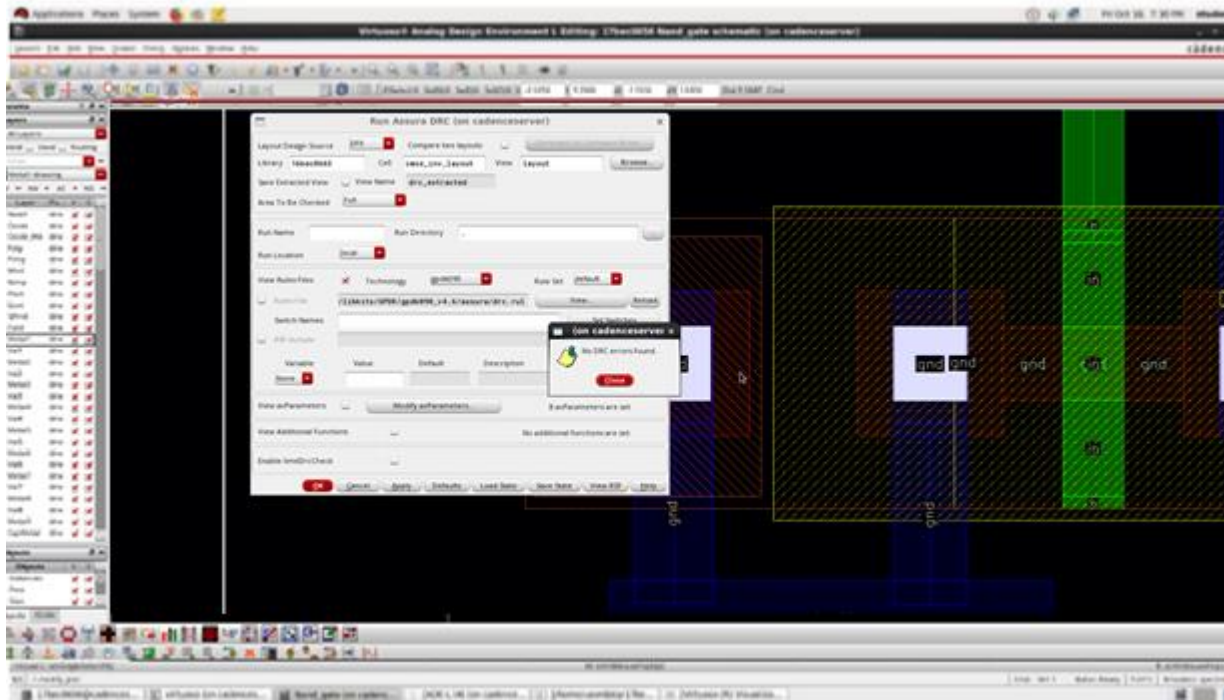


### 4. Removing LVS error

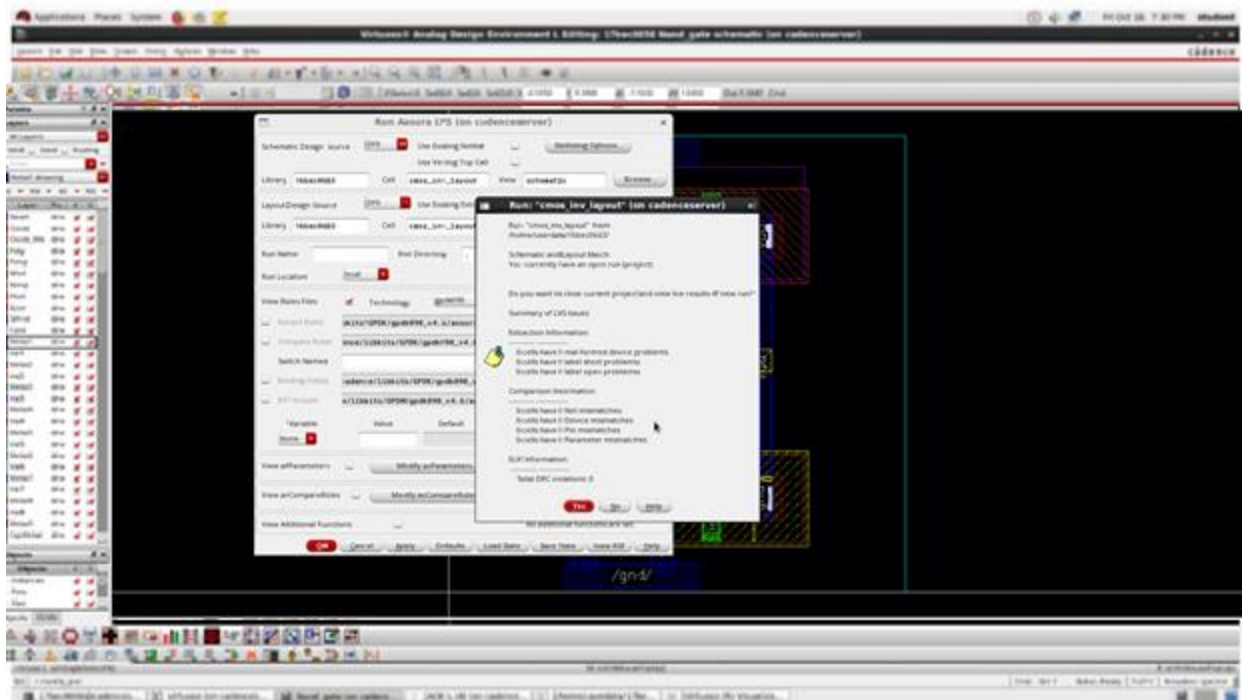


## 5. QRC check

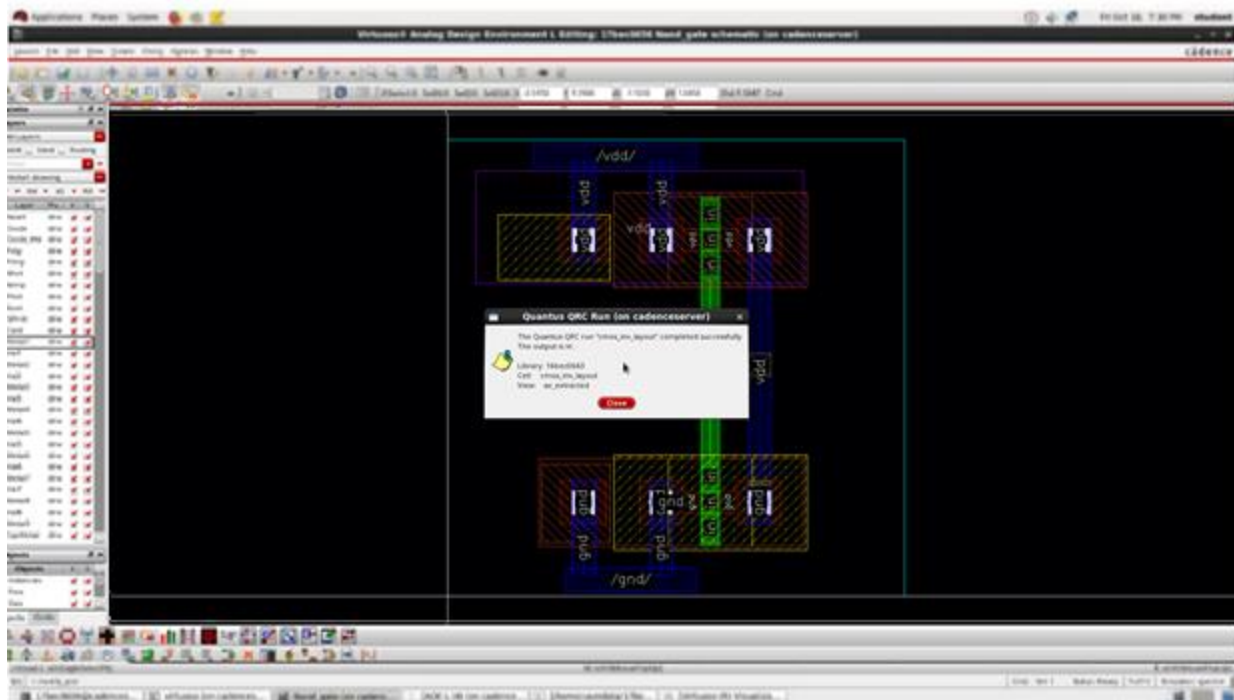


## 6. Testing

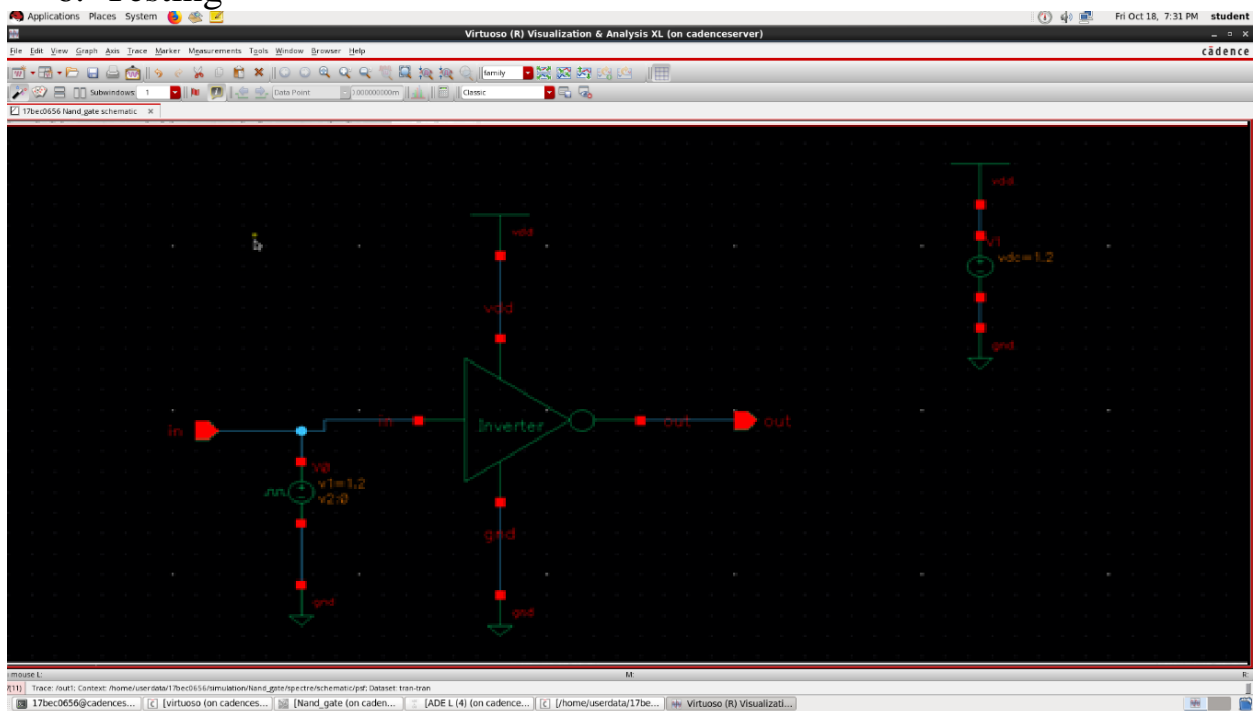
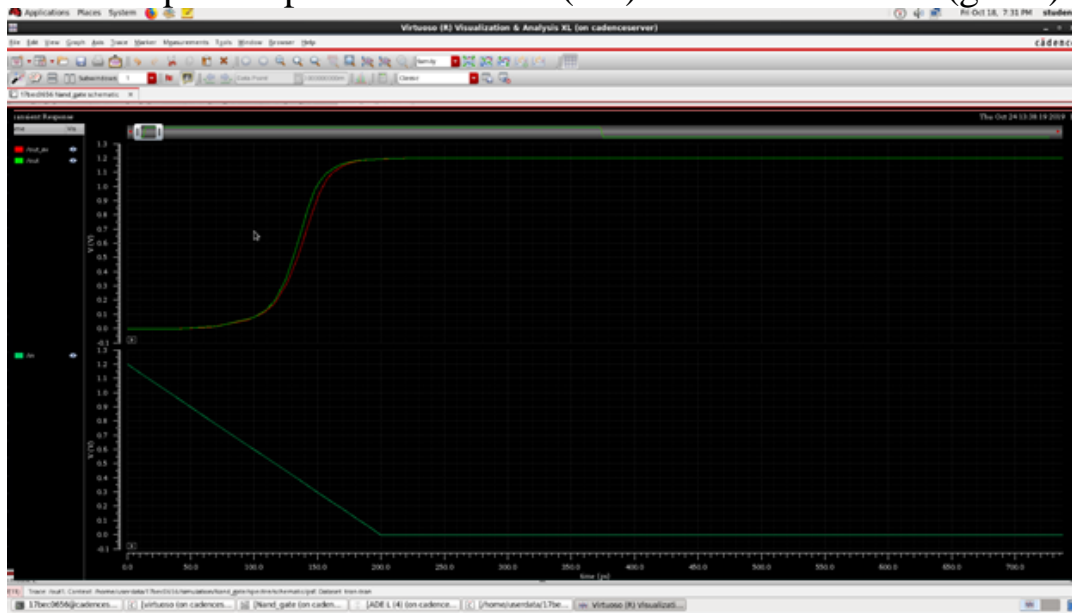
## 7. Output Graph b/w extracted (red) and non-extracted (green) outputs



## 8. Delay (Rising)

 

## 9. Delay (Falling)



## Calculations

### Rising

With AV extracted = 132.86 ns

Without AV extracted = 129.32 ns

Rising Delay = 3.54 ns

### Falling

With AV extracted = 22.191 ns

Without AV extracted = 22.028 ns

Falling Delay = 0.163 ns

## Results and Inference

Schematic and Layout of CMOS Inverter were successfully created and tested without any errors.

Rising Delay = 3.54 ns

Falling Delay = 0.163 ns

---